 


# Term Project ECE - 111


## Viterbi Decoder

1.

a. RTL schematic



b. Post mapping schematic

 


c. Resource usage

	Resource	Usage
1	▼ ALUTs Used	391 / 36,100 ( 1 % )
1	-- Combinational ALUTs	391 / 36,100 ( 1 % )
2	-- Memory ALUTs	0 / 18,050 ( 0 % )
3	-- LUT_REGS	0 / 36,100 ( 0 % )
2	Dedicated logic registers	255 / 36,100 ( < 1 % )
3		
4	▼ Combinational ALUT usage by number of inputs	
1	-- 7 input functions	8
2	-- 6 input functions	73
3	-- 5 input functions	16
4	-- 4 input functions	28
5	-- <=3 input functions	266
5		
6	▼ Combinational ALUTs by mode	
1	-- normal mode	215
2	-- extended LUT mode	8
3	-- arithmetic mode	168
4	-- shared arithmetic mode	0
7		
8	▼ Logic utilization	516 / 36,100 ( 1 % )
1	-- Difficulty Clustering Design	Low
2	▼ -- Combinational ALUT/register pairs used in final Placement	481
1	-- Combinational with no register	226
2	-- Register only	90
3	-- Combinational with a register	165
3	-- Estimated pairs recoverable by pairing ALUTs and registers as design grows	-38
4	▼ -- Estimated Combinational ALUT/register pairs unavailable	73
1	-- Unavailable due to Memory LAB use	0
2	-- Unavailable due to unpartnered 7 LUTs	8

\* Register count does not include registers inside RAM blocks or DSP blocks

#### d. Simulation (ZOOM IN TO SEE DATA)

## ENCODER

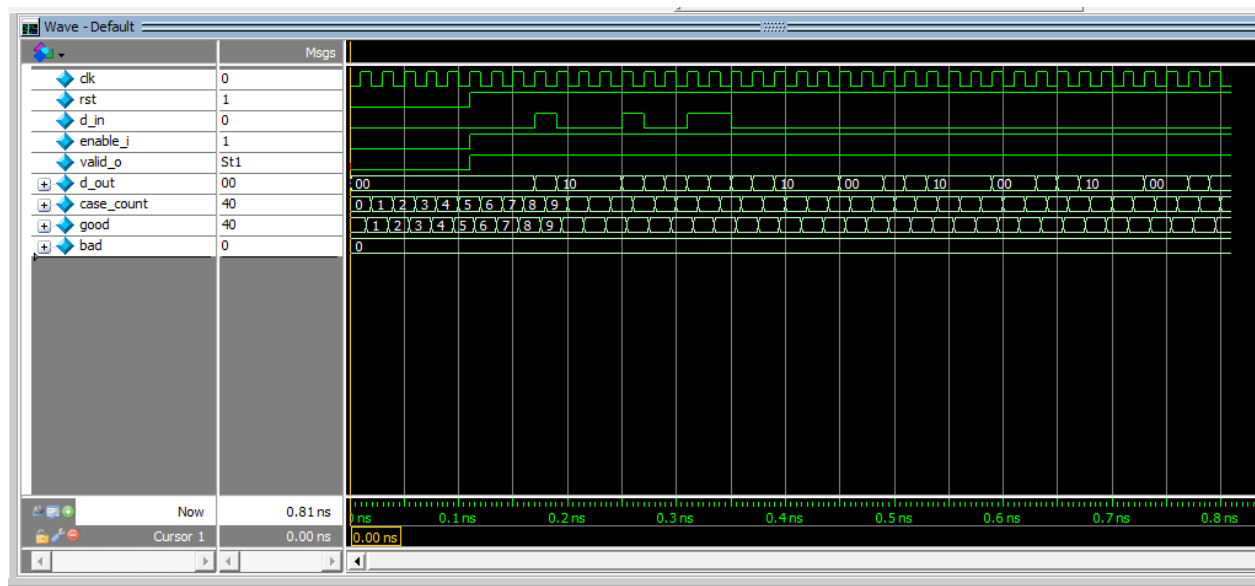


```
# yaa 0 10 10
# yaa 0 10 10
# yaa 0 00 00
# yaa 0 00 00
# yaa 0 10 10
# yaa 0 00 00
# yaa 0 10 10
# yaa 0 10 10
# yaa 0 10 10
# yaa 0 00 00
# yaa 0 00 00
# yaa 0 10 10
# yaa 0 00 00
# yaa 0 10 10
# yaa 0 10 10
# yaa 0 00 00
# yaa 0 00 00
# yaa 0 10 10
# yaa 0 00 00
# good = 40, bad = 0
# ** Note: $stop : C:/Users/Venz/Downloads/encoder/encoder/encoder_tb.sv(51)
# Time: 810 ps Iteration: 0 Instance: /encoder_tb
```

### Explanation (Encoder) -

Our Encoder is designed by using 8 case states. Depending on each current state a certain value is assigned to the next state concurrent with the state table for the encoder. As well as a d\_out\_reg. Then on the next clk or rst a value is assigned to current state. Either the next state for 3'b000.

## DECODER

 

```
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# yaa! in = 1, out = 1
# good =          256, bad =           0
# ** Note: $stop      : C:/Users/Venz/Desktop/ECE 111/HW8/vitassign/viterbi_tx_rx_tb.sv(371)
#    Time: 1381700 ps Iteration: 0 Instance: /viterbi_tx_rx_tb
# Break in Module viterbi tx rx tb at C:/Users/Venz/Desktop/ECE 111/HW8/vitassign/viterbi tx rx tb.sv line 371
```

### e. Verilog Design Code

**Github Repository - <https://github.com/Vnz01/ECE-111-HW-Assignments.git>**